

Cours 1: Notions de VHDL

I) Introduction


- VHDL :
Very high speed integrated circuit Hardware Description Language
- Langage de description de circuit et de tests de circuits
- Les éléments décrits fonctionnent simultanément, ce qui est très différent des langages séquentiels que vous connaissez!!!

I.1.a Description d'interconnexions

```
entity exemple is
  port ( A : in  std_logic;
        B : in  std_logic;
        C : in  std_logic;
        D : out std_logic);
end exemple;

architecture BEHAVIORAL of exemple is
  attribute BOX_TYPE : STRING ;
  signal S1 : std_logic;
  component XOR2
    port ( I0 : in  std_logic;
          I1 : in  std_logic;
          O  : out std_logic);
  end component;

   component AND2
    port ( I0 : in  std_logic;
          I1 : in  std_logic;
          O  : out std_logic);
  end component;
begin
  BLOC1 : XOR2
    port map (I0=>B, I1=>A, O=>S1);
  BLOC2 : AND2
    port map (I0=>C, I1=>S1, O=>D);
end BEHAVIORAL;
```



I.2.b Description de tests

```
LIBRARY IEEE; USE IEEE.STD_LOGIC_1164.ALL;
IEEE.NUMERIC_STD.ALL; USE IEEE.STD_LOGIC_TEXTIO.ALL;
USE STD.TEXTIO.ALL;

ENTITY testExSimple IS
END testExSimple;


BEGIN
A <= '0';
B <= '0';
C <= '0';
-----
WAIT FOR 100 ns;
A <= '1';
C <= '1';
-----
WAIT FOR 100 ns; -- Time=200 ns
B <= transport '1';
-----
WAIT FOR 100 ns; -- Time=300 ns
A <= transport '0';
-----
WAIT FOR 150 ns; -- Time=450 ns
```

II Description fonctionnelle

a. Description vue de l'extérieur (ENTITY)

- Nom
- Entrées et sorties


Exemple

 

II.2 Description d'un composant combinatoire

 a. Exemple simple

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY Exemple1 IS
Port ( a : in std_logic;
b : in std_logic;
c : in std_logic;
s : out std_logic );
end Exemple1;
architecture Behavioral of Exemple1 is
begin
s <= (a or b) and not c;
end Behavioral;
```



b. MUX 4 vers 1, 16 bits

```

library IEEE;
...
entity MUX4_1_16bits is
  Port(E0,E1,E2,E3 : in std_logic_vector(15 downto 0);
        SEL : in std_logic_vector(1 downto 0);
        S : out std_logic_vector(15 downto 0));
end MUX4_1_16bits;
architecture Behavioral of MUX4_1_16bits is
begin
  process (E0,E1,E2,E3,SEL)
  begin
    CASE SEL IS
      WHEN "00" => S <= E0;
      WHEN "01" => S <= E1;
      WHEN "10" => S <= E2;
      WHEN OTHERS => S <= E3;
    end case;
  end process;
end Behavioral;

```




SEL	S
00	E0
01	E1
10	E2
11	E3

c. Additionneur signé

```

library IEEE;
...
entity addsub16 is
  Port ( A : in std_logic_vector(15 downto 0);
        B : in std_logic_vector(15 downto 0);
        S : out std_logic_vector(15 downto 0);
        CARRY : out std_logic;
        OVERFLOW : out std_logic);
end addsub16;
architecture Behavioral of addsub16 is
  signal S_interne : std_logic_vector(16 downto 0);
  begin
    CARRY<=S_interne(16);
    S<=S_interne(15 downto 0);
    S_interne <= (A(15) & A) + (B(15) & B);
    OVERFLOW <= (A(15) AND B(15) AND NOT S_interne(15)) OR (NOT A(15)
    AND NOT B(15) AND S_interne(15));
  end Behavioral;

```

 


3. Bascule D

```

library IEEE;
...
entity basculeD is
  Port ( D : in std_logic_vector(15 downto 0);
        CLK,Reset : in std_logic;
        Q : out std_logic_vector(15 downto 0));
end basculeD;
architecture Behavioral of basculeD is
begin
  process (CLK,Reset)
  begin
    if (Reset='1') then
      Q<=(others =>'0');
    elsif (CLK'event and CLK='1') then
      Q<=D;
    end if;
  end process;
end Behavioral;


```

 



Reset	CLK	Q
1	X	0
0	Front	D
0	Cte	Qp

4 Automate

 - Exemple, détection de 101 avec recouvrement
- Etape 1 : Graphe



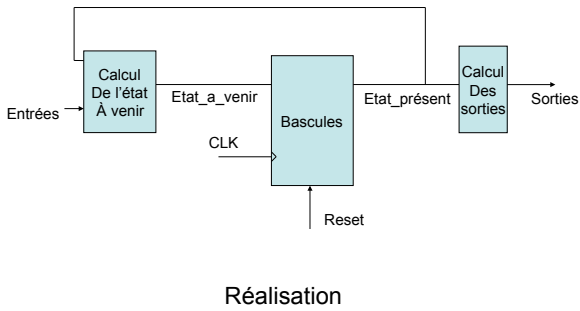

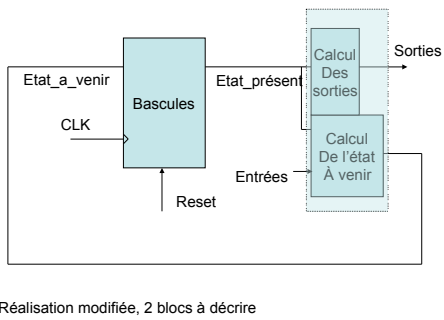

Description de l'entité :


```
library IEEE;
```

```
...
```

```
entity Detection101 is
```

```
  Port (
    e : in std_logic;
    CLK : in std_logic;
    RESET : in std_logic;
    s : out std_logic);
```

```
end Detection101;
```

 

Description du comportement

```
architecture Behavioral of Detection101 is
```

```
  type StateType is (debut,det1,det10,det101);
```

```
  signal ETAT_A_VENIR,ETAT_PRESENT : StateType;
```

```
begin
```

```
  BASCULES :
```

```
  process (CLK,RESET)
```

```
  begin
```

```
    if (RESET='1') then
```


```
      ETAT_PRESENT<=debut;
```

```
    elsif (CLK'EVENT AND CLK='1') THEN
```

```
      ETAT_PRESENT<=ETAT_A_VENIR;
```

```
    end if;
```

```
  end process BASCULES;
```

 

```
CALCUL_SORTIES_ET_ETAT_A_VENIR :
```

```
  process (ETAT_PRESENT,e)
```

```
  begin
```

```
    case ETAT_PRESENT is
```

```
      when debut =>
```

```
        s<='0';
```

```
        if (e='1') then
```

```
          ETAT_A_VENIR<=det1;
```

```
        else
```

```
          ETAT_A_VENIR<=debut;
```

```
        end if;
```

```
      when det1 =>
```

```
        s<='0'; ...
```

```
    end case;
```

```
  end process CALCUL_SORTIES_ET_ETAT_A_VENIR;
```

```
end Behavioral;
```

